

Total No. of Printed Pages:2

**SUBJECT CODE NO:- H-206**  
**FACULTY OF SCIENCE AND TECHNOLOGY**  
**S.E. (EC/ECT/IEC/E&C) (Sem-II)**  
**Electronics Devices & Circuits – II**  
**[OLD]**

[Time: Three Hours]

[Max. Marks:80]

N.B

Please check whether you have got the right question paper.

- 1) Q.1 from sections A and Q.6 from section B – are compulsory.
- 2) Solve any two questions from remaining questions from each section.
- 3) Assume suitable data wherever necessary.

## Section A


- |     |   |          |
|-----|---|----------|
| Q.1 | Solve any five questions  | 10       |
|     | <ol style="list-style-type: none"> <li>a) How power is dissipated in power amplifier?</li> <li>b) Draw the construction of IMPATT diode</li> <li>c) Explain working of LASER diode in brief</li> <li>d) What are ideal characteristics of op-amp?</li> <li>e) Draw I/P, O/P wave forms for class AB amp</li> <li>f) What is meant by push pull amplifier</li> <li>g) Give the different applications of BARITT diode</li> <li>h) Draw block diagram of operational amplifier</li> </ol> |          |
| Q.2 | <ol style="list-style-type: none"> <li>a) Draw and explain V-I characteristics of Tunnel diode</li> <li>b) What is meant by CCD? Explain</li> </ol>   | 08<br>07 |
| Q.3 | <ol style="list-style-type: none"> <li>a) Draw and explain transformer coupled amplifier</li> <li>b) Class – output stage has an efficiency of 60% if the maximum collector dissipation of each transistor is .5w, calculate the d.c input power and the a.c output power.</li> </ol>   | 08<br>07 |
| Q.4 | <ol style="list-style-type: none"> <li>a) Derive dual input dual output AC analysis of operational Amplifier</li> <li>b) Explain why pulse amplifier is needed draw its freq. domain response</li> </ol>  | 08<br>07 |
| Q.5 | Write short note on (any three) <ol style="list-style-type: none"> <li>a) Gunn diode</li> <li>b) Heat sink design</li> <li>c) Class-c amplifier</li> <li>d) Harmonic distortion in power amplifier</li> </ol>   | 15       |

## Section B

- |     |  |    |
|-----|--|----|
| Q.6 | Solve any five questions.  | 10 |
|     | <ol style="list-style-type: none"> <li>a) What is sweep generator?</li> <li>b) What is clamper? Draw input and output waveform for positive clamper.</li> <li>c) Explain in brief the role of commutating capacitor in self-biased binary.</li> <li>d) Differentiate between symmetric and asymmetric triggering.</li> <li>e) What is RC control blocking oscillator?</li> </ol> |    |

- f) What are basic types of sweep generators?
- g) What is diode control blocking oscillator?
- h) What is the effect of positive clipper circuit?

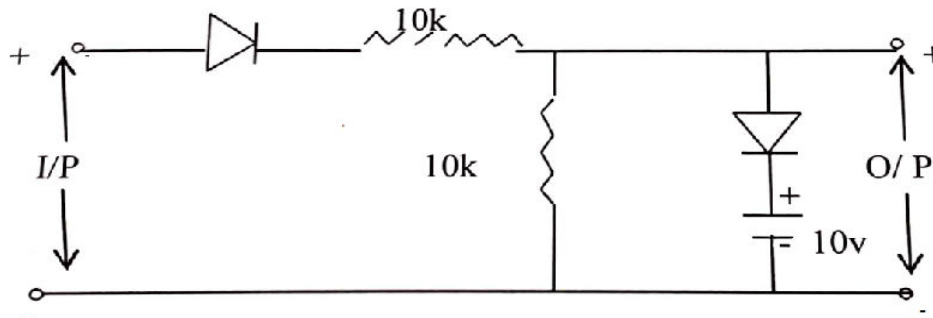- Q.7      a) What is the effect of positive biasing in positive clamper circuit?      08  
             b) Draw the frequency response of Differentiator for sine wave input.      07
- Q.8      a) Draw and explain AB Amplifier.      07  
             b) For the circuit shown below the input is  $50 \sin \omega t$ . draw the transfer characteristics and      08  
                 input output wave forms assuming ideal diodes



- Q.9      a) Draw and explain Monostable multivibrator      08  
             b) Draw and explain Miller's time base generator.      07
- Q.10      Write short note on ( any three )      15  
             a) RC controlled blocking oscillator  
             b) Boot strap sweep generator  
             c) current time base generator  
             d) Integrator