

Total No. of Printed Pages:03

**SUBJECT CODE NO:- H-1208**  
**FACULTY OF SCIENCE AND TECHNOLOGY**  
**S.Y.B.Tech. (ETC) (Sem-III)**  
**Electronics Devices & Circuits**  
**[OLD]**

[Time: Three Hours]

[Max.Marks: 80]


N.B

Please check whether you have got the right question paper.

- i. Q. No. 1 & Q. No. 6 are compulsory.
- ii. Attempt any two questions from the remaining questions in each section.

## Section A


- |     |  |          |
|-----|--|----------|
| Q.1 | Solve any five:  | 10       |
|     | <ol style="list-style-type: none"> <li>a) What is early effect?</li> <li>b) Define <math>\alpha</math> &amp; <math>\beta</math> of transistor.</li> <li>c) Enlist the types of biasing.</li> <li>d) What are the applications of h-parameters?</li> <li>e) What is bandwidth?</li> <li>f) Draw &amp; label frequency response of single stage CE amplifier.</li> </ol> |          |
| Q.2 | <ol style="list-style-type: none"> <li>a) How bias compensation is done in base bias with emitter feedback &amp; derive expression for <math>I_c</math>, <math>V_{CE}</math> &amp; <math>S</math>?</li> <li>b) Explain transistor as an amplifier.</li> </ol>  | 08<br>07 |
| Q.3 | <ol style="list-style-type: none"> <li>a) Explain the effect of emitter bypass capacitor on amplifier parameters.</li> <li>b) Compare h parameters of all configurations.</li> </ol>   | 08<br>07 |
| Q.4 | <ol style="list-style-type: none"> <li>a) For the single stage common collector amplifier circuit shown in figure. Calculate the value of <math>R_i</math>, <math>R_o</math>, <math>A_i</math> &amp; <math>A_v</math> <math>\beta = 100</math>, <math>V_e' = 2S/IE(MA)</math></li> </ol>   | 08       |

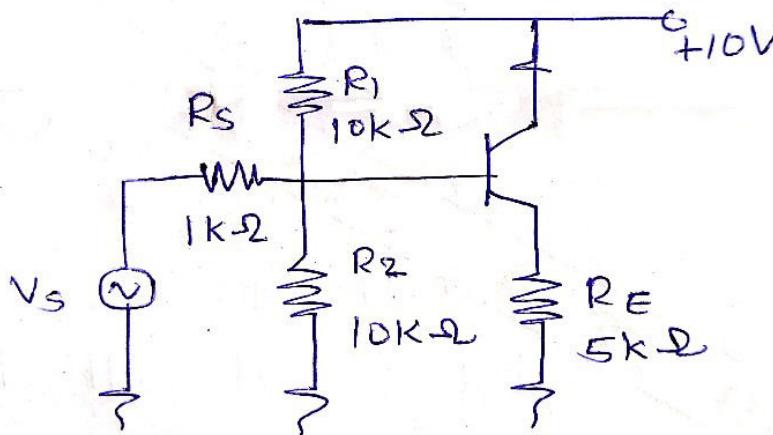

- b) Draw the equivalent circuit of CE amplifier in terms of h-parameter & obtain the expression for voltage gain. 07

Q.5

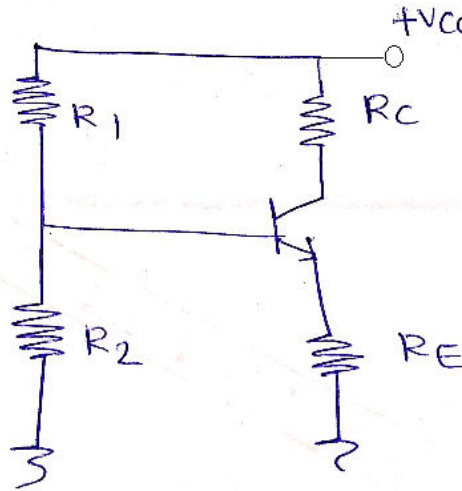- a) Derive the expression for the stability factor of a fixed bias. 07  
 b) Determine the values of resistances for the circuit shown in fig. such that  $I_c = 5\text{ mA}$ ,  $V_{CE} = 6\text{ V}$ ,  $V_c = 8\text{ V}$ ,  $S = 10$ ,  $\beta = 200$  &  $V_{cc} = 20\text{ V}$  08



## Section B

Q.6

Solve any five:

- Enlist the characteristics of class C power amplifier.
- What is the difference between voltage & power amplifier
- Derive relation between  $\mu$ ,  $gm$  &  $rd$ .
- Define Transconductance & give its unit.
- Draw & label the circuit diagram of common gate amplifier.
- What is inversion layer in E type MOSFET.


10

Q.7

- What are biasing schemes available to achieve the required bias in a JFET? Explain any one of the biasing schemes. 08
- Give the advantages & disadvantages of push pull configuration in power amplifiers. 07

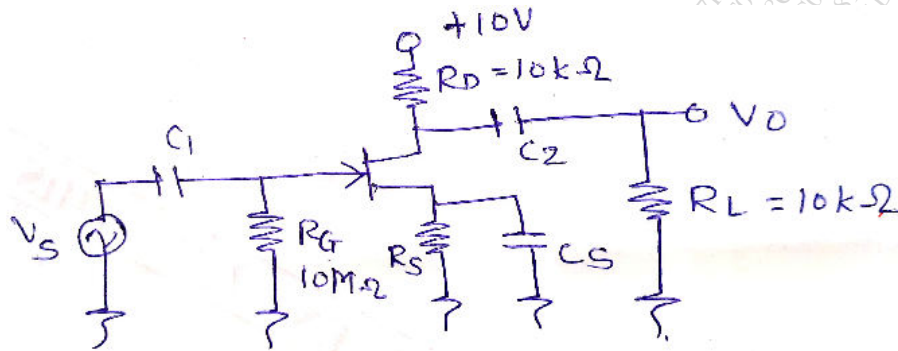Q.8

- Calculate the values of voltage gain input resistance & output resistance of the amplifier shown in fig. if  $gm = 4.2\text{ mA/V}$ ,  $r_D = 40\text{ k}\Omega$ . 08



b) Derive the expression for maximum conversion efficiency of class B power amplifier. 07

Q.9 a) Explain in detail V-MOSFET. 07

b) Explain depletion layer formation & operation of JFET. 08

Q.10 a) Draw drain characteristics of JFET & explain it. 08

b) Compare JFET & MOSFET. 07